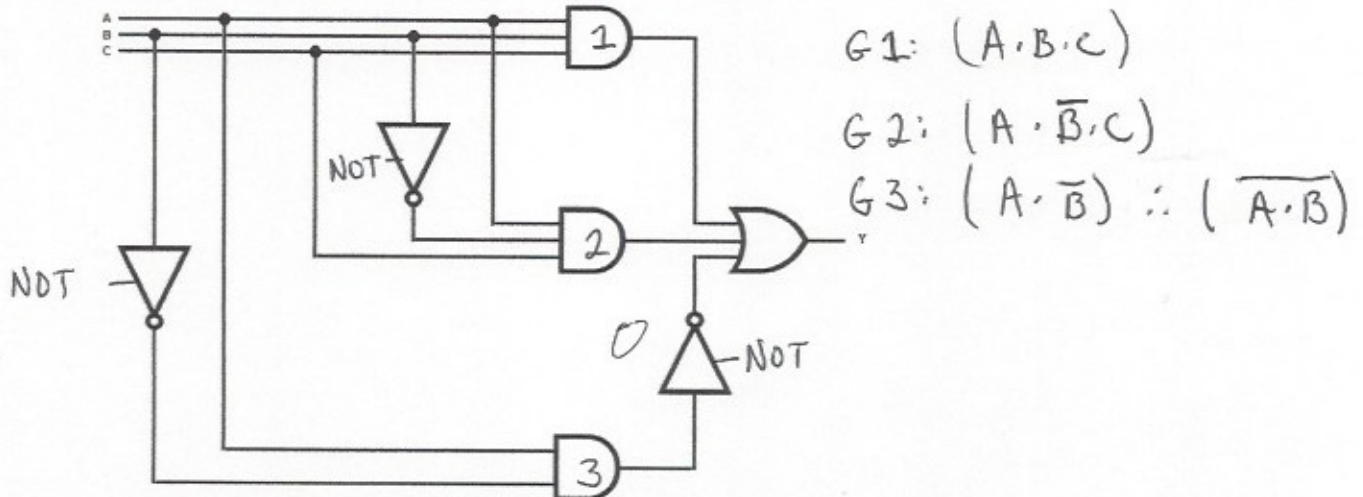


Author: Allen Myers
 Project: CIS021-HW Lab2
 Date: January 31st, 2019
 Module: CIS021-Homework 2
 Purpose: Convert a logic diagram to an output expression.
 Create truth tables.
 Minimize a circuit.

1. Examine the following circuit diagram:



2. Write the output formula for the diagram:

$$Y = (A \cdot B \cdot C) + (A \cdot \bar{B} \cdot C) + (\overline{A \cdot B})$$

3. Write the truth table for the formula produced in Step 2:

Y	A	B	C
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1

4. Reduce the circuit and write the new formula:

$$Y = (A \cdot B \cdot C) + (\bar{A} \cdot B) + (A \cdot \bar{B} \cdot C)$$

